

ECE 473 Lab 2 - Calculations, notes, questions

74HC138:

$I_L \text{ max} = 6\mu A$

Sink/source per pin: 25mA


$V_{CC} = 7(\text{max})$

- current of I/O ports → 40mA
- BJTs → use as switches (op as saturation)
- max ^{peak} op voltage - 6V
- forward current (from TEKboto datasheet) → 60mA
- continuous fwd current per seg (from tekdata datasheet) → 25mA
- each I/O port can sink 20mA @ $V_{CC} = 5V$
- Reverse current 100μA 10mA @ $V_{CC} = 3V$

$$I_C = \beta I_B \quad I_B = \frac{I_C}{\beta}$$

$$\frac{I_C}{I_B} = 100$$

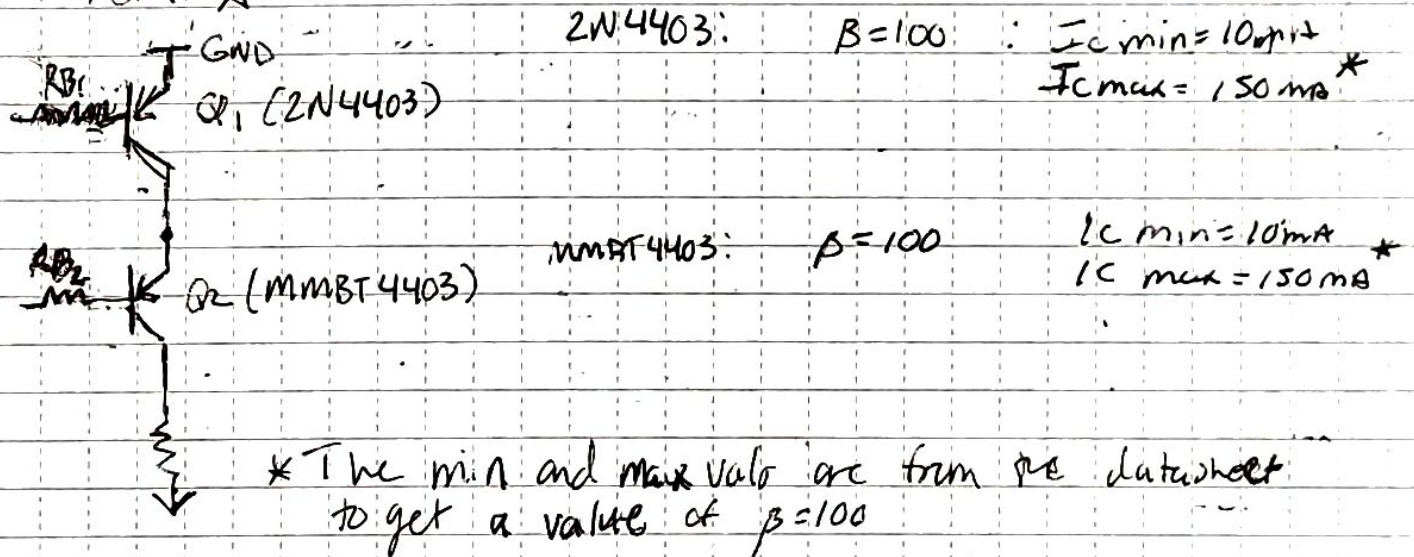- Each pin can sink 20mA of current
- The peak fwd current of each segment is 60mA
- The continuous fwd current of each segment is 25mA.
- We want to limit current to 20mA max running into Port A



1 SQUARE = _____


ECE 473 Lab 2 - calcs, notes, g's (contd.)

2N4403:
 $I_B = 2\text{mA}$
 $I_C = 80\text{mA}$
 $\beta = 100$

MMBT4403:
 $I_B = 2\text{mA}$
 $I_C = 80\text{mA}$
 $\beta = 10$

$$I_C = \beta I_B$$

$$I_B = \frac{I_C}{\beta}$$

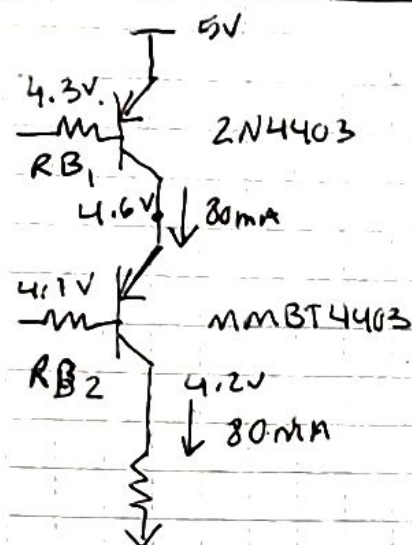

The display needs a continuous fuel current of 25 mA to power on per seg

max 8 segments on $10\text{mA} \times 8 = 80\text{mA}$

$$P_{wm} = 5V$$

MMBT4403: Given the desired I_C of 80 mA, according to the data sheet the I_B for "turn on" should be around 2 mA $V_{be} = 0.6 - 0.7$, $V_{ce} = 0.1V$

2N4403: $V_{ce\text{ sat}} = \sim 0.2\text{mA}$
 100 mA then $I_B = 1.0\text{mA} - 2\text{mA}$
 $V_{be} = \sim 0.75 - 0.9$

$$R_{30}: \frac{5V - 0.7}{2\text{mA}} \rightarrow \sim 2.2\text{k}\Omega \quad [2.1\text{k}\Omega \rightarrow 2.3\text{k}\Omega]$$

$$R_{29} = \frac{4.3 - 0.5}{2\text{mA}} \rightarrow \sim 2.2\text{k}\Omega \quad [2.1\text{k}\Omega \rightarrow 2.3\text{k}\Omega]$$

$R_1 - R_8$:

- Output of segments total (worst case) = 80 mA


- The max current the Ports can sink/supply = 20 mA

- $V_F = 1.8V$ for 10 mA $2.6V$ max drop per seg



$$\frac{4.3 - 2.06}{10\text{mA}} \rightarrow R_1 \dots R_8 = \sim 210 - 220\Omega$$

ECE 473 Lab 2 schematic

PORT B: "X" = NO CONNECT

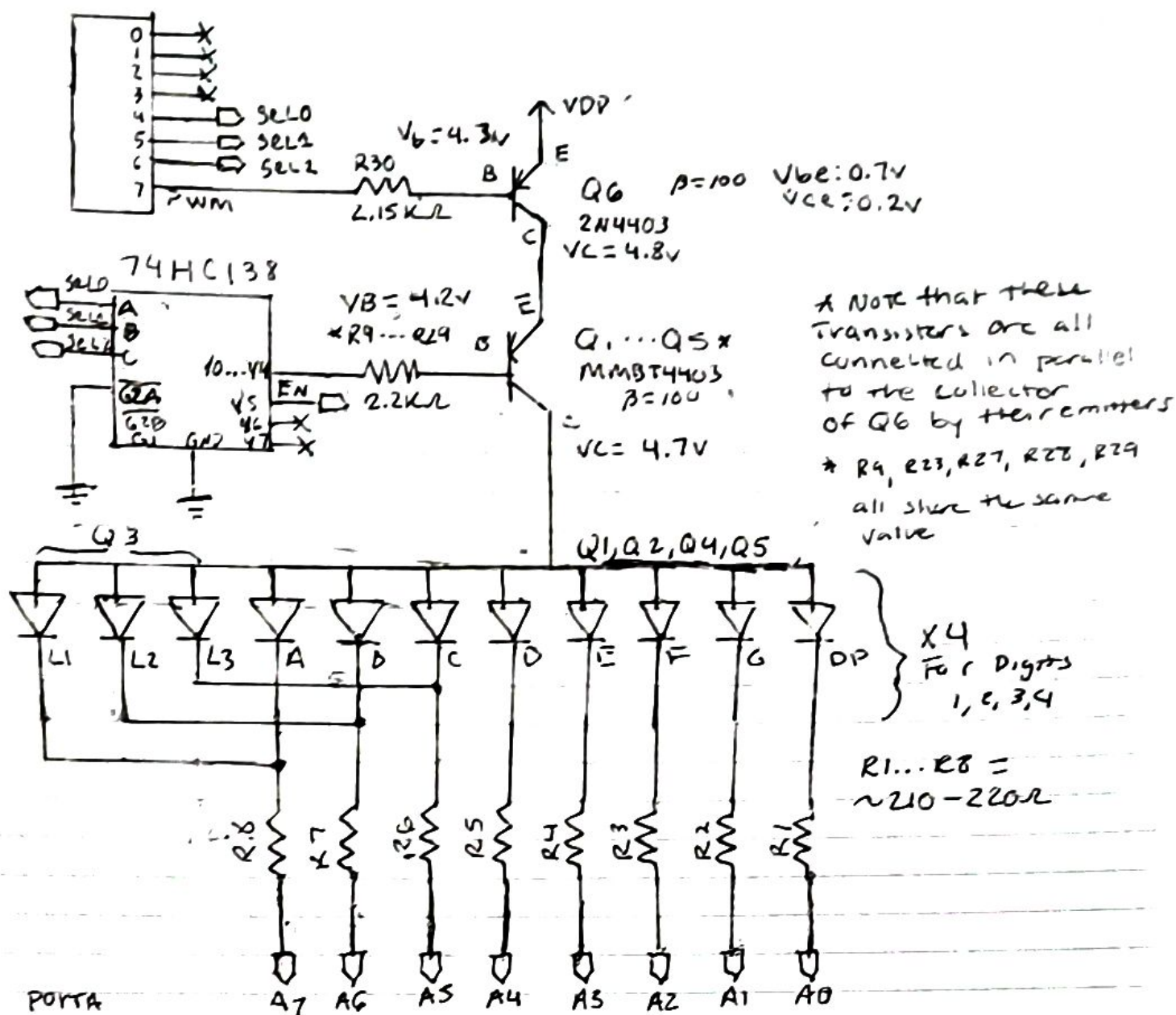

PORTA

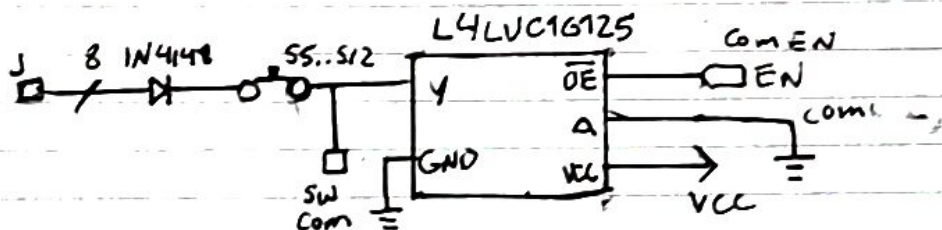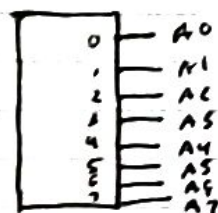

1 SQUARE =

ECE 473 Lab 2

- a) PORT A can sink a maximum of $.60\text{ mA}$ (20 mA per pin). In this case its not overloaded because at maximum the collector current to each pin should be around 10 mA according to my calculations (on the other pages :)).
- b) The current from the collector is within the forward current range ($10\text{--}20\text{ mA}$) needed to drive each segment on the display. Forward current is the necessary current to power on an LED. So since we met the forward current requirements, the segments will light (assuming the BJT stays in saturation.)
- c) In our case the tristate buffer is grounded through pin A. When $\overline{\text{OE}}$ is H and A is grounded the output is a high impedance off state. When $\overline{\text{OE}}$ is L and A is grounded the output to the switches is low. To allow to control the input on the $\overline{\text{OE}}$ pin, we can attach it to one of the unused outputs of the $74\text{HC}138$ decoder on the display board. We can toggle these outputs via the seg0, seg1, seg2 address pins.